

Problem 2.14

a)

$$f(w, x, y, z) = \sum (0, 2, 8, 10) + \sum_d (12, 14)$$

K-map:

| yz | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| wx 00 | 1 | | | 1 |
| 01 | | | | d |
| 11 | d | | | 1 |
| 10 | 1 | | | |

Minimal SOP:

$$f(w, x, y, z) = \bar{w} \bar{x} \bar{z} + w \bar{z}$$

b)

$$g(a, b, c, d) = \sum (5, 7, 13, 15) + \sum_d (6, 14)$$

| cd | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| ab 00 | | | | |
| 01 | | 1 | 1 | d |
| 11 | | 1 | 1 | d |
| 10 | | | | |

Minimal SOP:

$$g(a, b, c, d) = bd + b.c$$

$$[c] \quad h(w, x, y, z) = \Pi(0, 2, 8, 10) + \Pi_d(12, 14)$$

| $yz \backslash wx$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | 0 | | | 0 |
| 01 | | | | |
| 11 | d | | | d |
| 10 | 0 | | | 0 |

$$\text{pos of } h = (w+x+z)(\bar{w}+\bar{z})$$

$$\Rightarrow \text{dual of } h = (\bar{w} + \bar{x} + \bar{z})(w + z)$$

$$\Rightarrow \text{SOP of } h = (\bar{w} \cdot \bar{x} \cdot \bar{z}) + (w \cdot z)$$

$$\rightarrow \text{SOP of } h = w \cdot \bar{w} + w \cdot z + x \cdot \bar{w} + xz + z\bar{w} + z \cdot z$$

$$= \boxed{w \cdot z + x \cdot \bar{w} + xz + z\bar{w} + z}$$

$$[d] \quad t(a, b, c, d) = \Pi(5, 7, 13, 15) + \Pi_d(6, 14)$$

| $cd \backslash ab$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | 0 | 0 | d |
| 11 | | 0 | 0 | d |
| 10 | | | | |

$$\text{pos of } t = (\bar{b} + \bar{d})(\bar{b} + \bar{c})$$

$$\rightarrow \text{SOP of } t = \bar{b} \cdot \bar{b} + \bar{b} \cdot \bar{c} + \bar{d} \cdot \bar{b} + \bar{d} \cdot \bar{c}$$

$$= \boxed{\bar{b} \cdot \bar{c} + \bar{d} \cdot \bar{b} + \bar{d} \cdot \bar{c}}$$

Problem 2.24

Design POS expression for the 2-to-1 Mux in Fig 2.31

$$r(s, x, y) = \sum(1, 3, 6, 7)$$

Kmap:

| xy | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| s | 0 | 1 | 1 | — |
| 1 | — | — | 1 | 1 |

SOP expression: $r = \bar{s}y + sx$

$$\bar{r} = \overline{\bar{s}y + sx}$$

$$= (\overline{\bar{s}y}) \cdot (\overline{sx})$$

$$= (s + \bar{y}) \cdot (\bar{s} + \bar{x})$$


$$\text{SOP of } \bar{r} = \underbrace{s \cdot \bar{s}}_0 + s \cdot \bar{x} + \bar{y} \cdot \bar{s} + \bar{y} \cdot \bar{x}$$

$$= s \cdot \bar{x} + \bar{y} \cdot \bar{s} + \bar{y} \cdot \bar{x}$$

$$\text{Dual of } \bar{r} = (s + \bar{x})(\bar{y} + \bar{s})(\bar{y} + \bar{x})$$

POS expression of $r = (\bar{s} + x)(y + s)(y + x)$

Problem 2.27

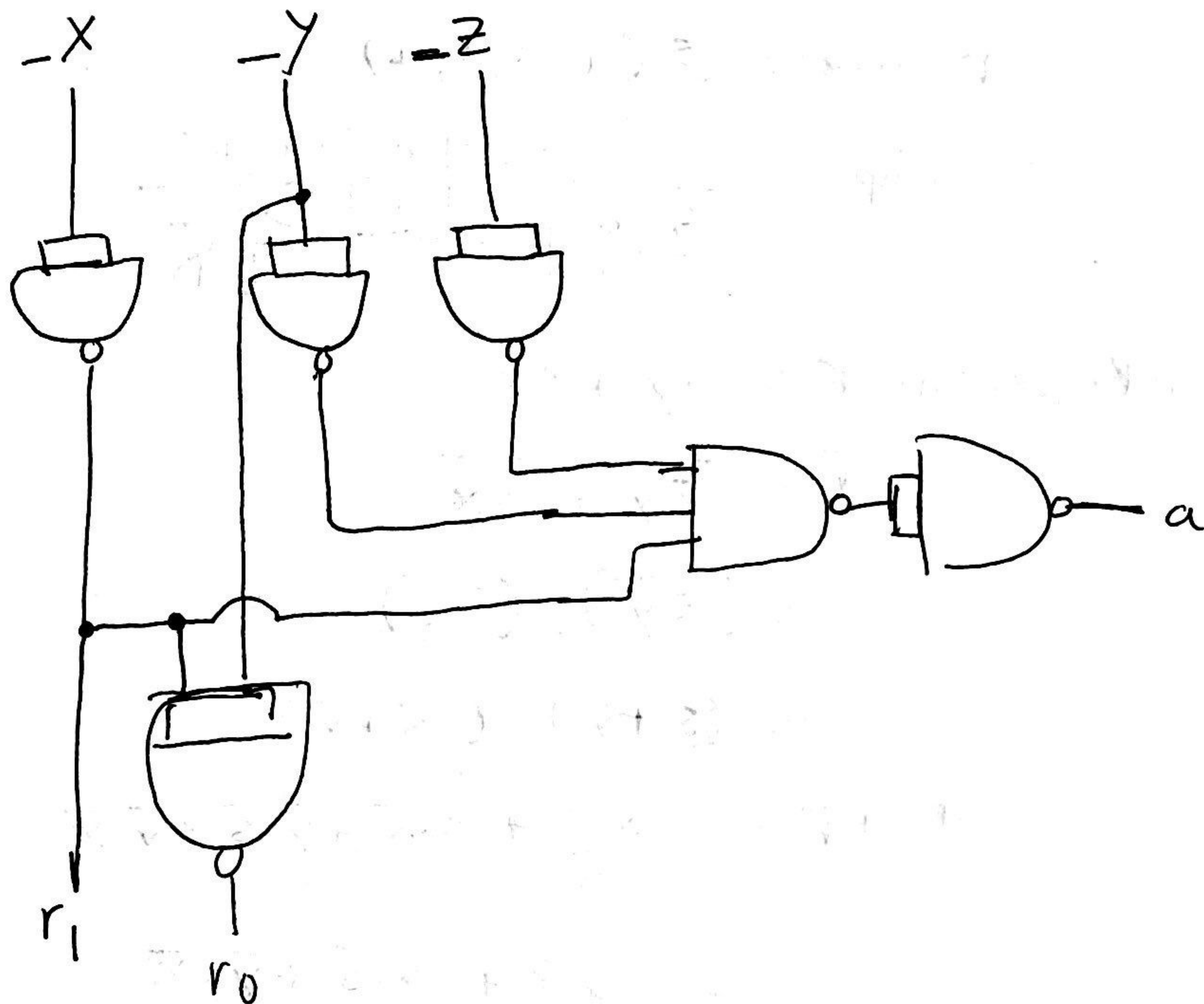

Problem 3.2

[a]

$$\begin{array}{r}
 A: 11001100 \\
 + B: 00110100 \\
 \hline
 \boxed{100000000}
 \end{array}$$

Carryout (not overflow bit)

[d]

$$\begin{array}{r}
 A: 11111000 \\
 B: 00001000 \\
 \hline
 ?
 \end{array}$$

$$\begin{array}{r}
 (B)_{1s} = 11110111 \\
 + 1 \\
 \hline
 -(B)_{2s} = 11111000
 \end{array}$$

$$\Rightarrow \begin{array}{r}
 A: 11111000 \\
 + B: 11111000 \\
 \hline
 \boxed{11110000}
 \end{array}$$

Carryout = 1 (not overflow bit)

[e]

$$\begin{array}{r}
 A: 10000010 \\
 - B: 00000011 \\
 \hline
 ?
 \end{array}$$

$$\begin{array}{r}
 (B)_{1s} = 11111100 \\
 + 1 \\
 \hline
 -(B)_{2s} = 11111101
 \end{array}$$

$$\Rightarrow \begin{array}{r}
 A: 10000010 \\
 + B: 11111101 \\
 \hline
 \boxed{10111111}
 \end{array}$$

Carryout = 1 (not overflow bit)

[f]

$$\begin{array}{r}
 A: 01111101 \\
 - B: 11111010 \\
 \hline
 ?
 \end{array}$$

$$\begin{array}{r}
 (B)_{1s} = 00000101 \\
 + 1 \\
 \hline
 -(B)_{2s} = 0000110
 \end{array}$$

$$\Rightarrow \begin{array}{r}
 A: 01111101 \\
 + B: 00000110 \\
 \hline
 \boxed{10000011}
 \end{array}$$

Problem 3.4

$$\Delta CPA(n) = (n-1) * \Delta FAC + \Delta FAS$$

With $\Delta FAC = 0.5ns$, $\Delta FAS = 0.3ns$


We have $\Delta CPA(8) = \Delta CPA(4) + \Delta CPA(4)$

$$= \left[(4-1)(0.5ns) + 0.3ns \right] + \left[(4-1)(0.5ns) + 0.3ns \right]$$


$$= 3.6ns$$

Problem 3.5


a)

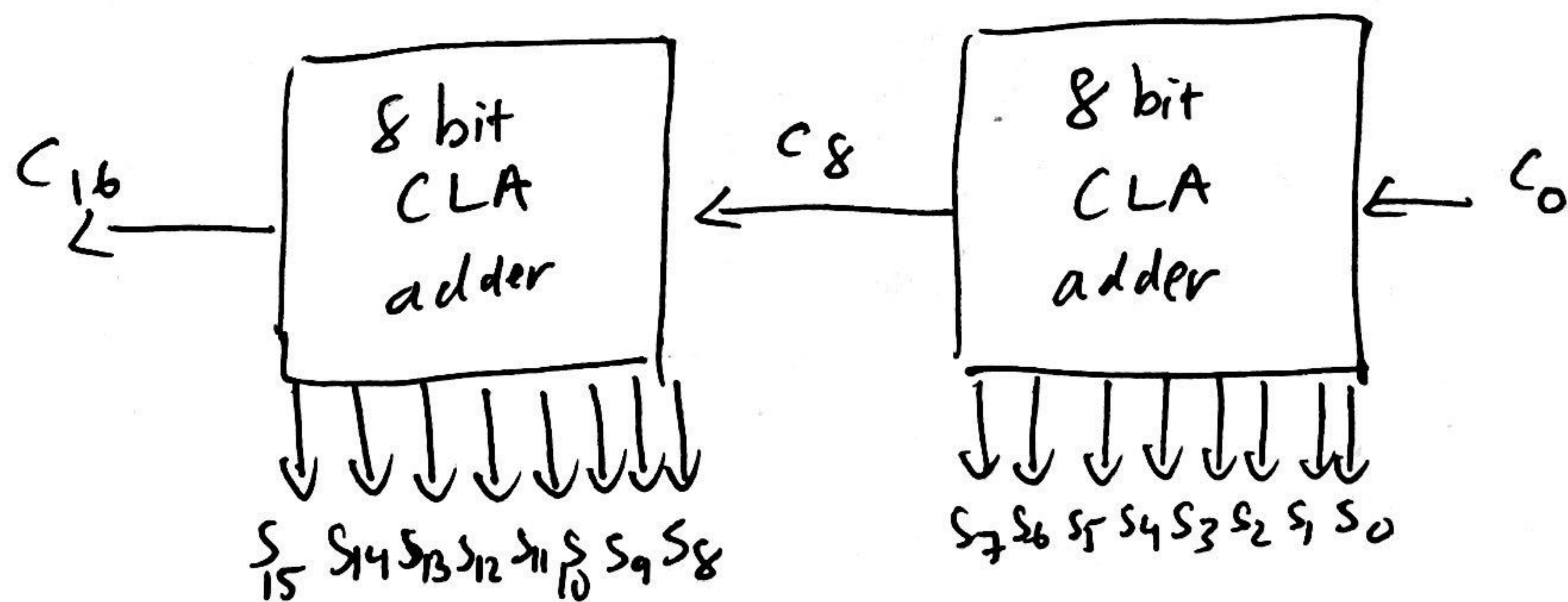

b)

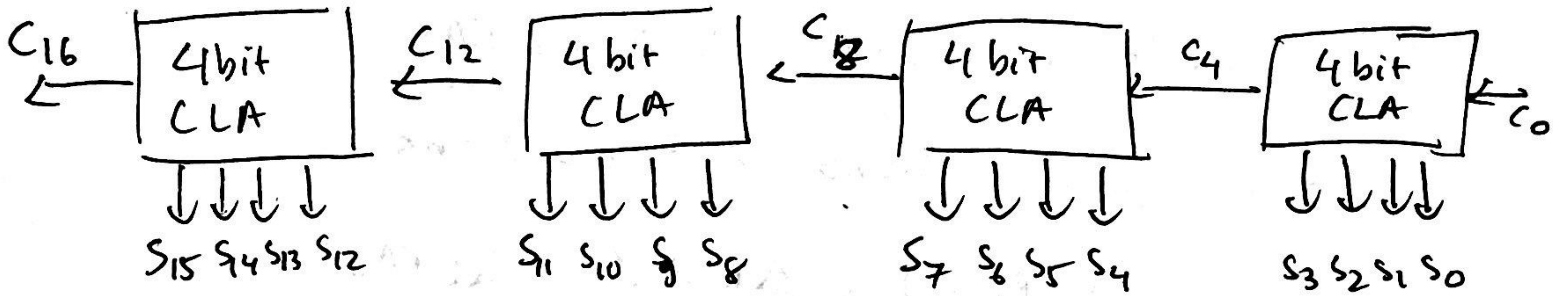

c)

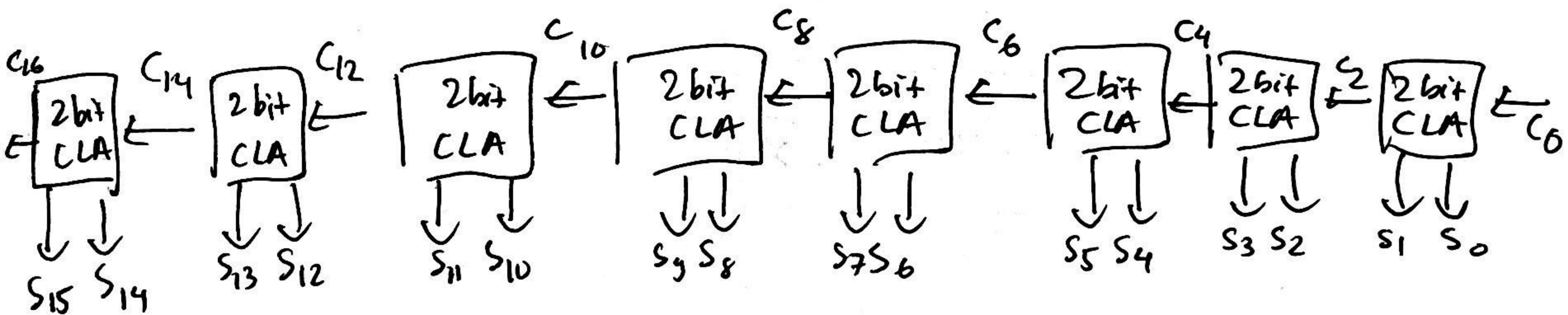


Problem 3.6

$$\text{Ratio of } \frac{\Delta CPA(8)}{\Delta CLA(8)} = \frac{1.7ns}{0.8ns} = 2.125$$


\Rightarrow The CLA(8) is more than 2 times faster than the CPA(8)

SOP expression for FA: $S_i = P_i \oplus C_{i-1}$

$$C_i = g_i + P_i C_{i-1}$$

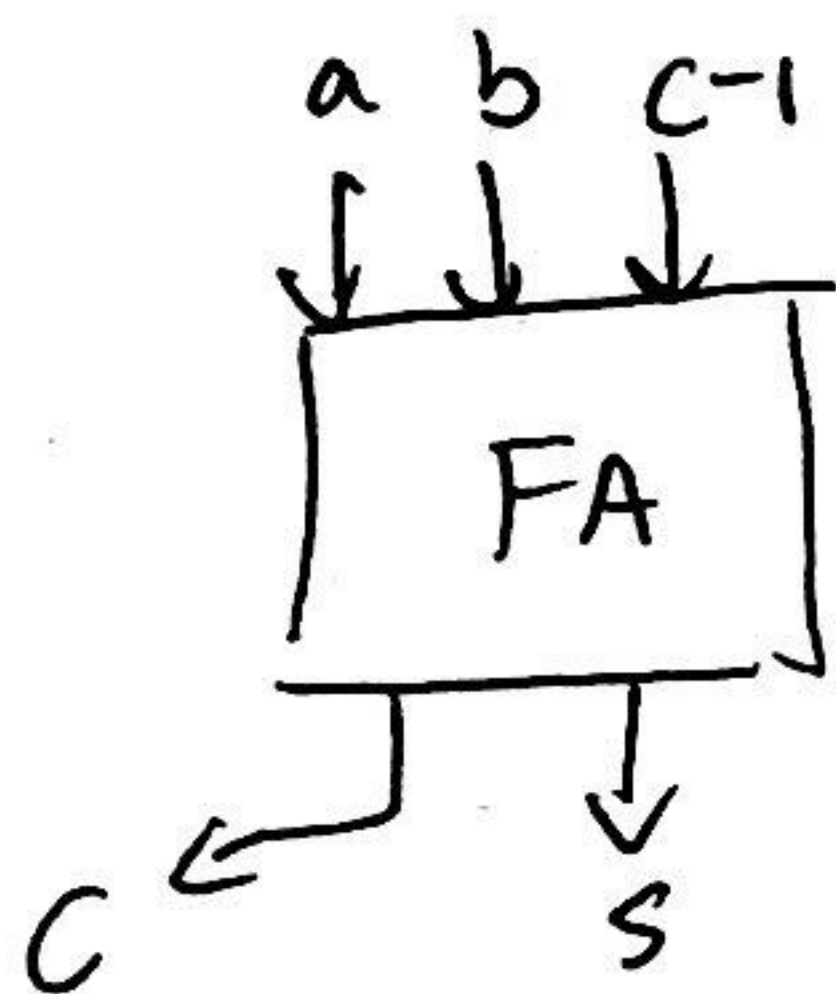

Problem 3.9

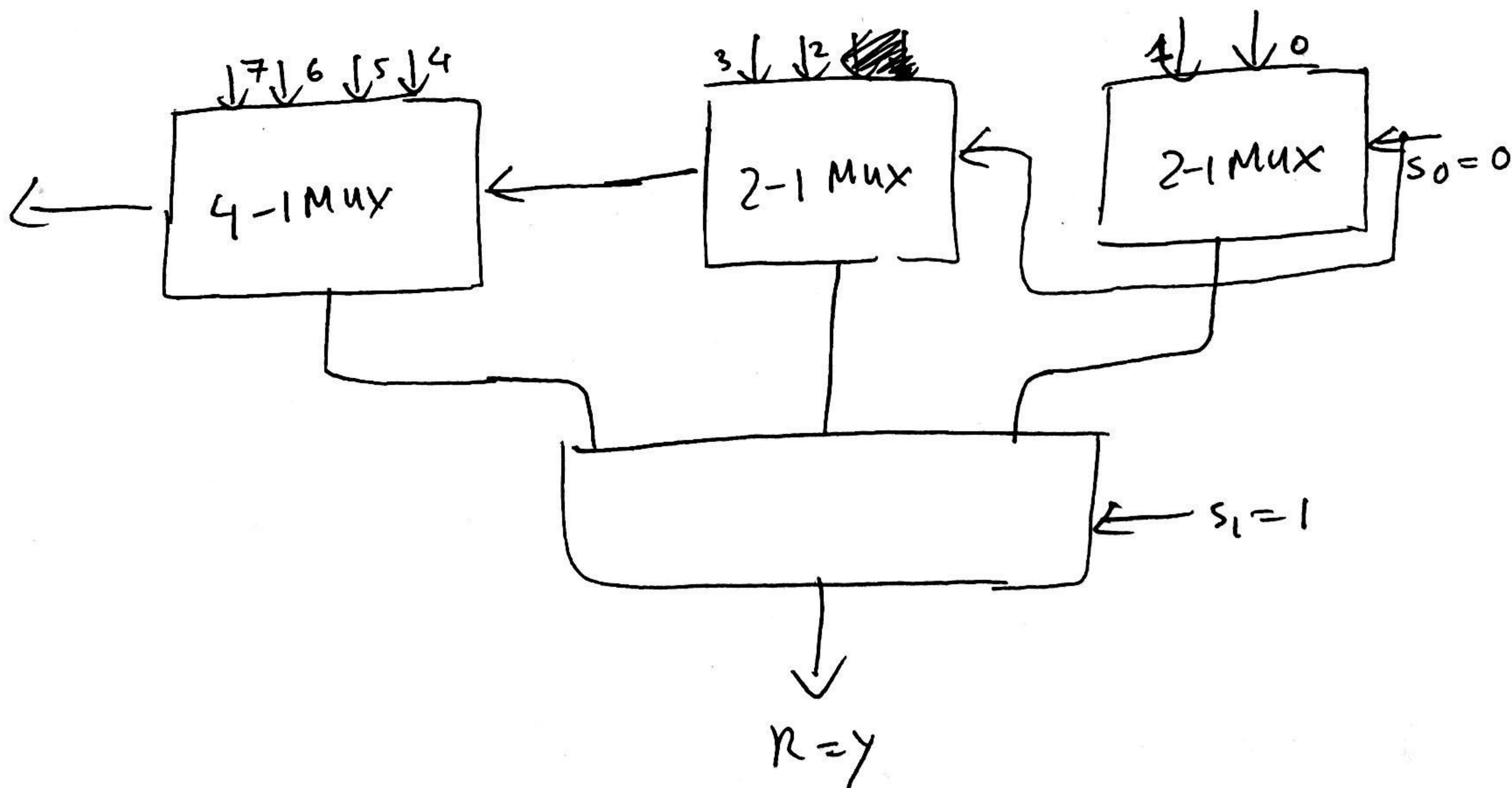

Problem 3.10

$$\Delta_{ALU}(8) = \Delta_{NAND} + \Delta_{OR} + \Delta_{MUX} + \Delta_{AM} \\ + \Delta_{MASK} + \Delta_{MAP}$$

$$= (0.1ns) + (0.8ns)$$

$$= 0.9ns$$

Problem 3.22

Represent 6.725 to IEEE Floating Point

a) Single Precision

$$6.725 = (110.1011100)_2$$

$$= (110.1011100)_2 \times 2^0$$

$$= (1.101011100)_2 \times 2^2$$

$$= (1.101011100)_2 \times 2^{2+127}$$

$$= (1.101011100)_2 \times 2^{129}$$

⇒ Sign 1 bit = 0

⇒ 8 bit biased exponent $E = 129 = (1000\ 0001)_2$

⇒ 23-bit fraction $F = 1010\ 11100\ 1100\ 1100\ 1100\ 11$

⇒

IEEE Floating Point:

| | | |
|---|-----------|------------------------------|
| 0 | 1000 0001 | 1010 11100 1100 1100 1100 11 |
|---|-----------|------------------------------|

or in hex:

0x40D73333

b)

$$6.725 = (110.1011100)_2$$

$$= (110.1011100)_2 \times 2^0$$

$$\cancel{= \cancel{110}} = (1.10101100)_2 \times 2^2$$

In double precision: $\text{bias} = 1023$

$$\Rightarrow (1.101011100)_2 \times 2^2$$

$$= (1.101011100)_2 \times 2^{2+1023}$$


$$= (1.101011100)_2 \times 2^{1025}$$

↳ Sign bit = 0

e7 11 bit biased exponent $E = 1025 = (100\ 0000\ 0001)_2$

t7 52 bit fraction F = 1010111001100110011001100110011001100110011001100.

⇒ IEEE Floating Point:

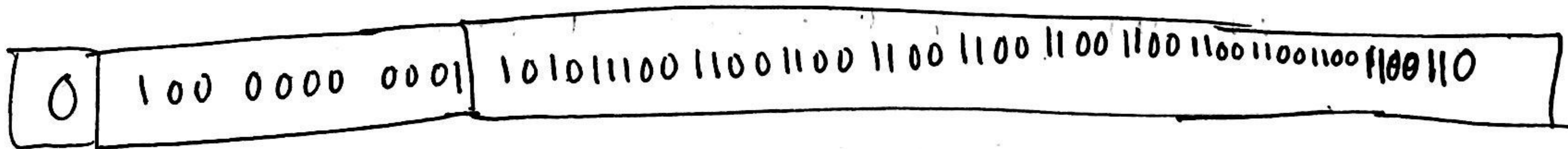

Problem 3.24

Represent IEEE single precision FP $0x41000000$ in decimal

$0 \times 41DD\ 0000$
 $\swarrow \quad \downarrow \quad \searrow \quad \searrow \quad \searrow$
 $0100 \quad 0001 \quad 1101 \quad 1101 \quad 0000 \quad 0000 \quad 0000 \quad 000$

$\Rightarrow (0, 100000011, 101110100000000000000000)$

with single precision, we have bias = 127

The biased 8 bit exponent $= (10000011)_2 = 131$

Exponent = $\frac{(biased\ exponent - bias)}{2}$

$$\text{So, } (1.1011101)_2 \times 2^{131} = (1.1011101)_2 \times 2^{4+127}$$

$$= (11011101)_2 \times 2^4 = (11011.101)_2 \times 2^0$$

$$11011.101 = 27 + (0.1)_2 + (0.001)_2$$

$$= 27 + \frac{1}{2} + \frac{1}{8}$$

$$= 27 + 0.5 + 0.125$$

Decimal = 27.625

Decimal